

Microprocessor Lab-work #2.2

7-segment LEDs

100-11-14

[1] Subject and goals

- (a) The access of six 7-segment LED for ON/OFF and pattern control in the 7-segment LED module
- (b) Organized display patterns in static or dynamic form can be achieved as required.

[2] Preparations

(a) Refer to the ckt schematic diagram:

- (a.1) how the 7-segment LED module may operate (its inputs to module for individual 7-seg LED selection as well as display pattern)?
- (a.2) functions of 7447 and BJT-2N3906 (discrete bipolar-transistor)?
- (a.3) data path from 51CPU to the 7-seg LED module?

(b) Datasheets reading:

- (b.1) TTL7447

(c) Readiness evaluation:


The 7-seg LED module physically consists of six 7-seg LED components, each being powered by a BJT acting as a power switch.

Can you or can you not

- (c.1) check the 7-segment LED module to see if it's working or not by manual wiring the circuitry?
- (c.2) write the codes for any static/dynamic pattern display on the module?
- (c.3) describe the operational limits of the 7-seg LED module imposed by the circuitry?


[3] **Lab-work for all:**

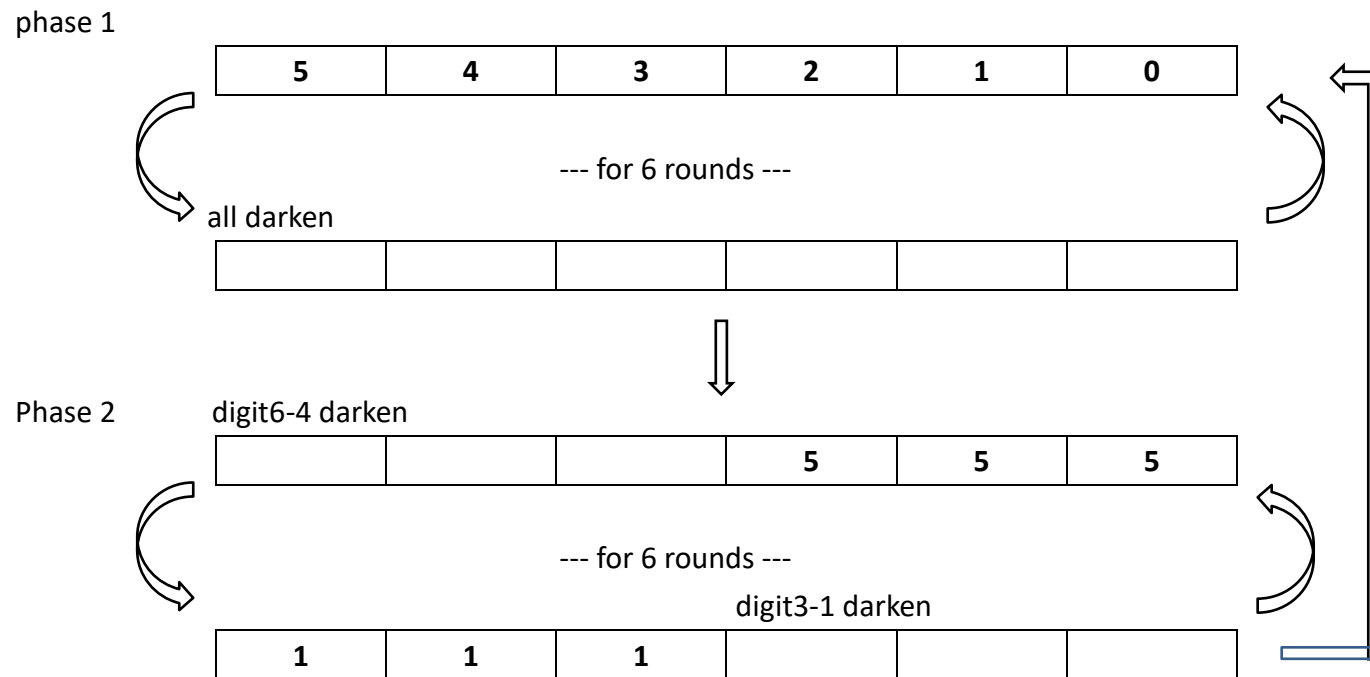The task here is to use the 7-seg LED module for the dynamic display sequence as graphically depicted below



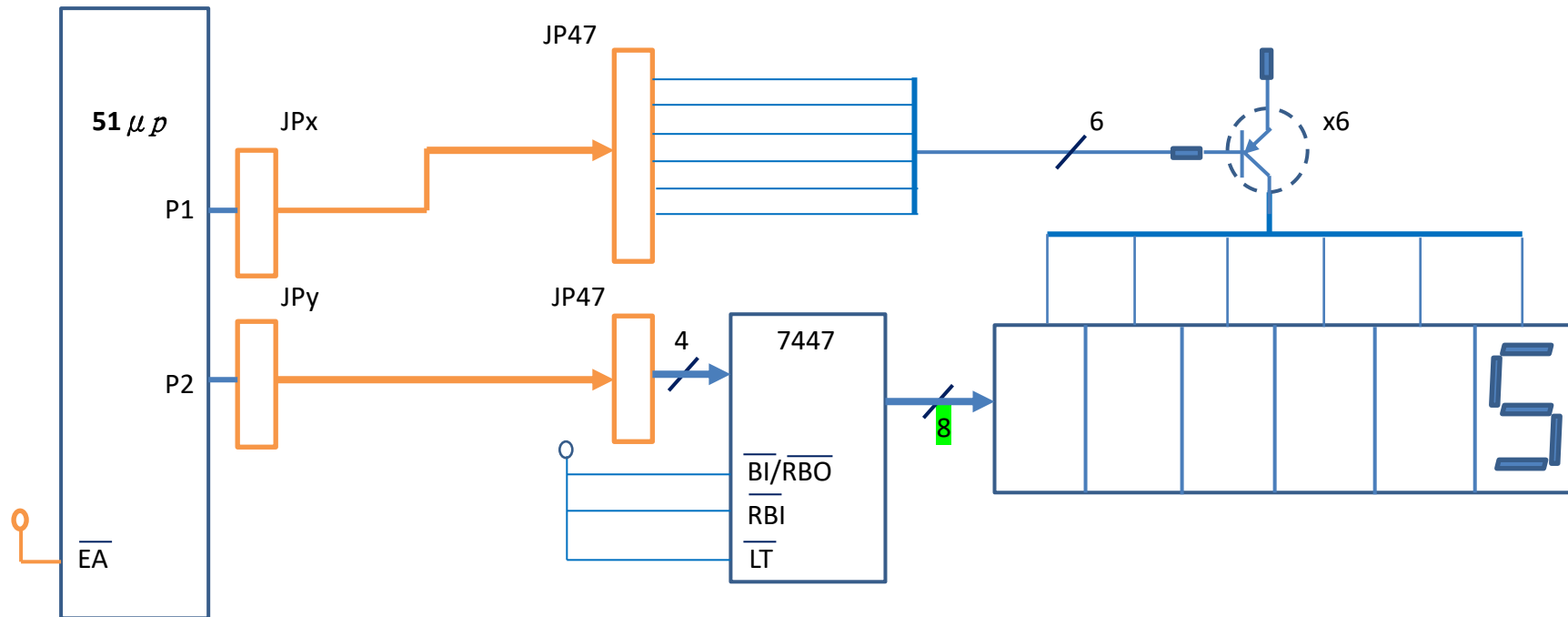(a) **Operating Procedure**

(a.1) **jumper-wiring for ckt setup** [refer to the schematic circuit diagram for wiring details]



(a.2) **code preparation:**

** edit the following sample 51 assembly code

** get the code ready for execution under IDE51 emulation

```

        org      0
        mov      SP, #50H
start:   mov      R7, #6
next1:
        mov      R5, #250
next11:
        mov      R6, #6
        mov      R1, #0FEH
        mov      R2, #0
next12:
        mov      A, R1
        mov      P1, A
        RL       A
        mov      R1, A
        mov      A, R2
        inc      R2
        mov      P2, A
        call     delay1      ; ===KKK===
        djnz     R6, next12
```

```

        djnz     R5, next11
        mov      P1, #0FFH
        call     delay2      ; ===LLL===
        djnz     R7, next1
        mov      R7, #6
next2:
        mov      P1, #0F8H
        mov      P2, #5
        call     delay2      ; ===III===
        mov      P1, #0C7H
        mov      P2, #1
        call     delay2      ; ===JJJ===
        djnz     R7, next2
        jmp      start
delay1:
        push     1
        mov      R1, #200
        djnz     R1, $
        pop      1
```

<pre> ret delay2: ; appx. 0.5sec delay, why? push 1 push 2 push 3 mov R1, #100 dd22: mov R2, #250 dd21: mov R3, #10 </pre>	<pre> djnz R3, \$ djnz R2, dd21 djnz R1, dd22 pop 3 pop 2 pop 1 ret end </pre>
--	---

** The sample code guarantees neither syntax err-free nor runtime err-free. Fix all syntax errs due to typo or whatever causes.

(a.3) **task execution:**

** start IDE51, download sample code (in HEX file format) from code preparation step (a.2)

** start execution and trouble-shooting if necessary

(b) Observations

(b.1) Is the code running well? Why or why not?

(b.2) What may happen to the display if the instruction marked by **===III===** being omitted? Why so? And what about the consequence of omitting the line marked by **===JJJ===**? And **===LLL===**?

(b.3) Is the delay provided by **delay1** appropriate considering execution time balance between the 4 phases? Too short? Too long?

(b.4) What might happen if the *R1-push* and *R1-pop* instructions are omitted in **delay1**? And the omitting of *push-pop* instructions in **delay2**?

(b.5) Can you modify the code so as to make it shorter, quicker, in better code structure or smoother execution?

[4] Comprehension evaluation:

- (a) If the code line marked by ===KKK=== are removed, do you still see the pattern 5-4-3-2-1-0 **VERY** clearly? Explain why so or not so.
What would you expect to see if the delay offered by **delay1** is made 1000 times of the original value?
- (b) Do the code lines marked by ===KKK=== actually resolved the problem in [4](a)? With the circuitry unchanged, could the problem be solved purely by S/W measure alone? Suppose the problem could be really remedied by a small modification on the circuitry, what would it be?

[5] Designated Assignment

Let $k = \text{mod}(T, 6)$, where T is the table# in the laboratory. Please fulfill the assignment given in Q (**k**).

- Q(0) Manually wire-up the circuit so that all 7-seg digits display “0”, without code-driving. Rewire the circuit so that “0” appears on digit-0, and again without code-driving. Explain the difference in the display intensity perceived in the two cases.
- Q(1) Do the same as in (0), except for “1” appearing respectively on all digits and on digit-1 alone.
- Q(2) Do the same as in (0), except for “2” appearing respectively on all digits and on digit-2 alone.
- Q(3) Do the same as in (0), except for “3” appearing respectively on all digits and on digit-3 alone.
- Q(4) Do the same as in (0), except for “4” appearing respectively on all digits and on digit-4 alone.
- Q(5) Do the same as in (0), except for “5” appearing respectively on all digits and on digit-5 alone.