

NCTU-CS Digital System Lab.

Lab06 Decode ALU(DALU)

Data Preparation

Use and learn **ISE tool and ChipScope Pro** to accomplish this design, and make sure you are familiar with tool and setting:

1. Download Lab06.zip from e3 platform.
2. Use ISE tool to run Simulation.
3. Program your code (DALU.v) on Spartan 3E to view Wave by **ChipScope Pro**.

Design Description and Examples

An arithmetic logic unit (ALU) is a digital electronic circuit that performs arithmetic and bitwise logical operations on integer binary numbers. In this Lab, a string of instructions will be given. Your job is to decode these instructions and execute. You should try to design a simple ALU. The basic required instruction are following:

Type	- Format – (19-bits)			
L	opcode(3-bits)	ssssss(6-bits)	ttttt (6-bits)	func (4-bits)
O	opcode(3-bits)	ssssss(6-bits)	ttttt (6-bits)	llll (4-bits)
I	opcode(3-bits)	ssssss(6-bits)	iiiiiii (10-bits)	

L: logic O: operation I: 10bits number operation

A instruction[18:0] can be divided into few parts as above.

ssssss, ttttt, llll, iiiiii represent the 6bits and 4bits and 10bits signed numbers, respectively. Decode the opcode & func by the following rule to compute answer.

In this Lab, there are 19bits instructions meaning 19bits numbers. TA will offer testbench containing a counter to count $0 \sim 2^{19}-1$ and assign in **instruction[18:0]** to check your design.

Function Name	Meaning	Type	Instruction Binary Encode
AND	ssssss & ttttt (bit-wise)	L	000-ssssss-ttttt -0000
OR	ssssss ttttt (bit-wise)	L	000-ssssss-ttttt -0001
XOR	ssssss ^ ttttt (bit-wise)	L	000-ssssss-ttttt -0010
ADD	ssssss + ttttt	O	000-ssssss-ttttt -0011
SUB	ssssss – ttttt	O	000-ssssss-ttttt -0100
Mult	ssssss * ttttt * llll	O	001-ssssss-ttttt -llll
Square	(ssssss + ttttt + llll)^2	O	010-ssssss-ttttt -llll
ADDI	ssssss + iiiiiiii	I	011-ssssss -iiiiii-iiii
SUBI	ssssss – iiiiiiii	I	100-ssssss -iiiiii-iiii

P.s.: llll are LLLL not 1111

Input :

instruction[18:0]: 001 000011 000001 0011

Mult: 3*1*3 = 9

Output :

9

You should output 9 in 1 cycle with out_valid high.

Your goal is to compute these operations by above rules and output the correct answer.

Inputs

1. **instruction[18:0]** is valid while **in_valid** is high.
2. All inputs will be changed at clock *negative* edge.
3. All operations are signed.

Input Signals	Bit Width	Description
clk	1	Positive edge trigger clock
rst	1	active-high synchronous reset
instruction[18:0]	19	19 bits input
in_valid	1	high when instruction[18:0] is valid



Outputs


1. Your answer should be output at **out[15:0]** in only **1 cycle**
2. **out [15:0]** is signed integer.
3. **out_valid** should be low and **out** should be set to zero after initial reset.
4. **out_valid** should be set to high when output value is valid.
5. All outputs are synchronized at clock **positive** edge.
6. Test pattern will check whether your answer is correct or not at clock **negative edge** when **out_valid** is high.

Output Signals	Bit Width	Description
out [15:0]	16	out[15:0] are synchronous to the positive edge
out_valid	1	high when out[15:0] is valid

Specifications

4. Top module name : **DALU** (File name : **DALU.v**)
5. Input pins: **clk, rst, in_valid, instruction[18:0]**.
6. Output pins: **out_valid, out[15:0]**.
7. **out_valid** should not be raised when **in_valid** is high (when **in** data is transferring).
8. It is **active-high synchronous** reset.
9. **All operations are signed.**
10. Grading policy:
 1. RTL(40%)
 2. Program your code on Spartan 3E(20%)
 3. Use tool at TA demo time(30%)
 4. Question(10%)

Block Diagram

 

Note

1. Use ISE tool to run Simulation.
2. Program your code on Spartan 3E to view Wave by **ChipScope Pro**.
3. Please add your student ID and name to the file name of .v file before upload file on e3 platform:
DALU_0556123_陳小明.v
4. Sample waveform:

