

Microprocessor Lab-work #3uVision

4x4 Keypad Scanning

100-11-14

[1] Subject and goals

- (a) interconnecting structure of a 4x4 keypad, together with scanning and encoding process
- (b) balance among several IO-control tasks that have to be executed in order repetitively

[2] Preparations

(a) Refer to the ckt schematic diagram:

- (a.1) how the DIP switch, 4x1 switch, and 4x4 keypad module(s) would be scanned.
- (a.2) data path(s) from 51CPU to the target switch module(s)?

(b) Datasheets reading:

- (b.1) none

(c) Readiness-evaluation:

Can you or can you not

- (c.1) check if the target module (i.e., any switch and any 7-seg LED digit) is working properly or not by manually wiring the circuitry?
- (c.2) carry out trouble shooting along the path way when the lab-work isn't going as expected? How will you do that?

[3] Lab-work for all:


(a) Operating Procedure

TASK 1 encoding for any single key entry during 4x4 keypad scanning and then displaying the key-code on the 7-seg LED module, respectively with one and two 7-seg digit(s)

** 4x4 keypad set up ** code preparation ** code executing under IDE51 emulation

- (a.1) jumper-wiring for 4x4 keypad module setup

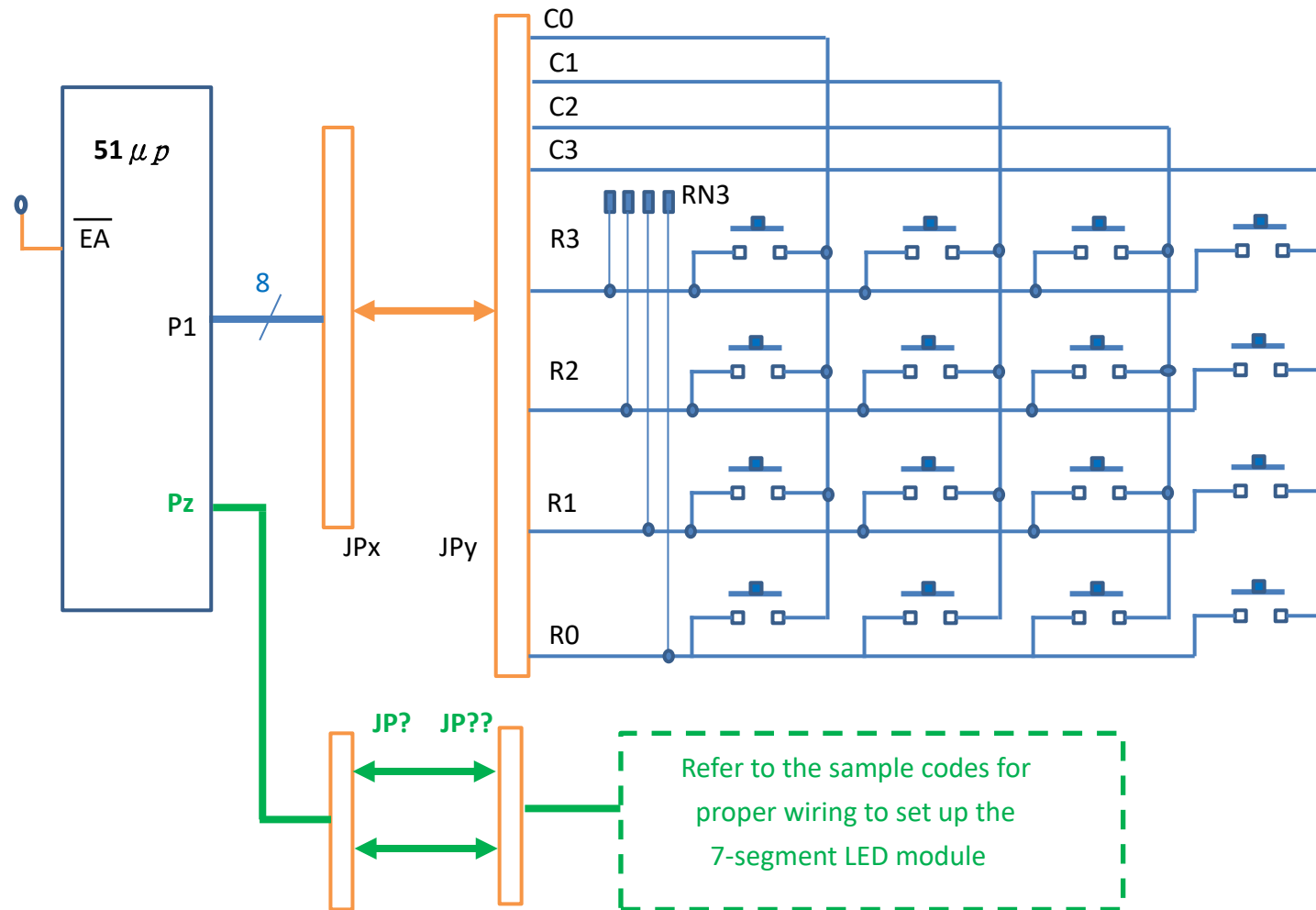Refer to the schematic circuit diagram, do all jumper-wiring necessary for setting up the circuitry as required below.



(a.2) code preparation:

** edit the following sample 51 assembly codes, ...two versions

** get version1 codes ready for execution first, then version2

```

; =====
; version 1 key-code display on one 7-seg
;      digit
;      x  x  x  x
;      8  9  x  x
;      4  5  6  7
;      0  1  2  3
;      Xs: non-decimal 7-seg patterns
; =====
; port 1 for keypad scanning
; P1: 0-3 output for column scanning
; P1: 4-7 input for row reading
; port 2 for using one digit of 7-seg LED
      org 0
      mov sp, #50H
      mov P2, #0FFH
col0:  mov R6, #0
      mov P1, #0FEH
      mov A, P1
col1:  mov R6, #1
      mov P1, #0FDH
      mov A, P1
      orl A, #0FH
      swap A
      cpl A
      jnz keycoding
col2:  mov R6, #2
      mov P1, #0FBH
      mov A, P1
      orl A, #0FH
      swap A
      cpl A
      jnz keycoding
col3:  mov R6, #3
      mov P1, #0F7H
      mov A, P1
      orl A, #0FH
      swap A
      cpl A
      jz col0
keycoding: ; A: 0-9,A,B,C,D,E F
      rr A
      anl #0FH
      jnb A.2, cont
      mov A, #3
cont:  jz cont2
      mov R7, A
      clr A
cont1: add A, #4
      djnz R7, cont1
cont2: add A, R6
display: ; when A>9 ???
      oal A, #0E0H

```

```

mov    P2, A
jmp    col0
; =====

```

```

; =====
; version 2 key-code display on two 7-seg
;      digits
;      12  13  14  15
;      08  09  10  11
;      04  05  06  07
;      00  01  02  03
; =====

```

```

; port 1 for keypad scanning
;   P1: 0-3 output for column scanning
;   P1: 4-7 input for row reading
; port 2 for using two digits of 7-seg LED

```

```

    org    0
    mov    sp, #50H
    mov    R7, #15
    mov    P2, #0FFH
col0:  mov    R6, #0
    mov    P1, #0FEH

```

```

                                end
                                ; =====

                                mov    A, P1
                                cpl    A
                                jnz    keycoding
                                call    display    ; ==??==
col1:  mov    R6, #1
    mov    P1, #0FDH
    mov    A, P1
    orl    A, #0FH
    swap   A
    cpl    A
    jnz    keycoding
    call    display    ; ==??==
col2:  mov    R6, #2
    mov    P1, #0FBH
    mov    A, P1
    orl    A, #0FH
    swap   A
    cpl    A

```

```

                                jnz    keycoding
                                call    display    ; ==??==
col3:  mov    R6, #3
    mov    P1, #0F7H
    mov    A, P1
    orl    A, #0FH
    swap   A
    cpl    A
    jz     col0
kecoding:  ; A: 0-9,A,B,C,D,E F
    rr     A
    anl    #0FH
    jnb    A.2, cont
    mov    A, #3
cont:    jz     cont2
    mov    R7, A
    clr    A
cont1:  add    A, #4

```

	djnz	R7, cont1	orl	A, #0D0H	push	3	
cont2:	add	A, R6	mov	P2, A	mov	R2, #20	
	mov	R7, A	call	delay	xxx:	mov	R3, #250
	call	display ; ==??==	mov	A, B	djnz	r3, \$	
	jmp	col0	anl	A, #0FH	djnz	r2, xxx	
display:			orl	A, #0E0H	pop	3	
	push	PSW	mov	P2, A	pop	2	
	push	A	call	delay	ret		
	push	F0H ; push B??	pop	F0H			
	mov	A, R7	pop	A	end		
	mov	B, #10	pop	PSW	; =====		
	div	A, B	ret				
	anl	A, #0FH	delay: push	2			

(a.3) task execution:

- ** start IDE51 emulator for the execution of code version1 and observe circuit behaviors
- ** start IDE51 emulator for the execution of code version2 and observe circuit behaviors
- ** start trouble-shooting if necessary

[**Key:** checking along the data path in a stage by stage manner, from the start: inside of 89c51 to the end: the target modules.]

(b) Observations

(b.1) Is code version 1 or version 2 running well? If so, it's a night of yours.

If not, congratulate you that you have a chance for getting more experience in trouble-shooting.

(b.2) While running version 1 sample code, one 7-seg LED will show the key-code when a key is entered and the display would remain so until the next entry of a key. For each key-code display, how many times does 89c51 access the 7-seg LED digit? And how many

times of accesses occur in between two key entries? What does that tell about the output nature of P2?

- (b.3) Consider the limits imposed by the 7-seg LED module, what could you say regarding the issue of handling both keypad scanning and the display of two 7-seg LEDs concurrently?
- (b.4) Instead of jumping to the label **display** as done in version 1 sample, version 2 sample code deals with two 7-segment LED digits showing different patterns by calling the subroutine **display**. Why? Is there a better approach to placing the call instructions other than at the lines marked by **==??==** in version2 code lines?
- (b.5) Without **RN3** pull-up resistor array, will the keypad module still function properly? Why or why not?
- (b.6) As the code of version 2 starts up, "15" appears on the two 7-seg LED digits even before key entry. Fix the problem!
- (b.7) Elongate the duration of **delay** in version2 sample code by 10 times of its original setting. What do you see regarding the change in circuit behaviors? Explain.

[4] Comprehension evaluation

- (a) Could you modify version-1 codes for a shorter code length or a better coding structure (e.g., handling 4-column scanning with a loop-body)?
- (b) How could the version-2 codes be revised in such a way that the handling of the display of two 7-seg LEDs and keypad scanning would be resolved somewhat more elegantly?
- (c) Consider the duration of a typical key entry from the moment of key pressing to that of key releasing, how long would it be? When a key is entered while executing either version of the sample codes, how many times the CPU would have detected this very same key entry? What are the issues to be tackled in coding such that one-detection for one-entry could be achieved?
- (d) Consider the case of multiple key entry in which more than one keys are pressed at one time. Could you write the codes using the 4x1 switch module, where each switch is assigned an value, say 1, 2, 3 and 4 respectively, for summing up values resulting from multiple key entry and displaying the sum on any of the 3 LED modules on the circuit board?