

NCTU-CS Digital System Lab.

Online Test 01

Data Preparation

1. Extract LAB data from TA's directory.
`% tar xvf ~2016dlabtestta05/Online_Test1.tar`

Design Description and Examples


Design two mode:

Input :

In: A_0 A_1 B_0 B_1

Mode 0 :

Four inputs A_0, A_1, B_0, B_1 which get from **in** port by 4 cycles are 16-bits **signed complex numbers**. For each input, the former 8 bits are the real part of each number and last 8 bits are the image part otherwise. Two parts of this complex number, real part and image part, all are **twos-complement representation**. First two inputs belong to A series, and the last two inputs belong to B series, otherwise.

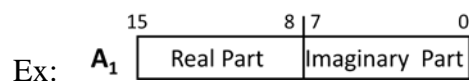

You should complex conjugate A series first, and convolute with B series then.

$$\bar{A} \circ B = \sum_{k=-\infty}^{\infty} \bar{A}_k * B_{n-k}$$

$0 \quad \bar{A}_0 \quad \bar{A}_1$	$\bar{A}_0 \quad \bar{A}_1$	$\bar{A}_0 \quad \bar{A}_1$
$\times \times \times$	$\times \times$	\times
$B_1 \ B_0 \ 0$	$B_1 \ B_0$	$B_1 \ B_0$

Output : $\bar{A}_0 \ B_0$ $\bar{A}_0 \ B_1 + \bar{A}_1 \ B_0$ $\bar{A}_1 \ B_1$

Model1:

You should cut each input a **set of 4 bits**. Each set is representing the range of 4bits numbers: 0~15. Find the maximum and minimum set and output sequentially **max**, **min value** and **max minus(-) min** in 3 continuous cycles:

A₀: 1111_0100_1101_1101 A₁: 1011_1101_0101_0011
B₀: 1000_0010_1000_0100 B₁: 0001_1010_0110_1001



A₀:

1111	0100	1101	1101
------	------	------	------

 A₁:

1011	1101	0101	0011
------	------	------	------

B₀:

1000	0010	1000	0100
------	------	------	------

 B₁:

0001	1010	0110	1001
------	------	------	------

Output : Max: **15**(1111) Min: **1**(0001) Max – Min: **14**

You should output sequentially in 3 continuous cycles : 15 1 14

Your goal is to compute these operations by above rules and output the correct answer.

Inputs

1. Four input data for **in[15:0]** each will be sequentially input in **4 continuous** cycles while **in_valid** is high.
2. **in_mode** valid at the *first* input cycle.
3. All inputs will be changed at clock *negative* edge.

Input Signals	Bit Width	Description
clk	1	clock
rst_n	1	synchronous active-high reset
in	16	4 of 16 bit inputs
in_valid	1	high when in is valid
in_mode	1	select the operations should be compute by two MODE discuss above

Outputs


1. Your answer should be output at **out[35:0]** for **only 3 cycle** when **MODE = 0**; Whereas, output at **out[35:0]** for **only 3 cycle** when **MODE = 1**.
2. For **mode 0**, **out[35:0]** is signed complex number, also. The former 18 bits are the real part, and last 18 bits are the image part otherwise.
3. For **mode 1**, **out[35:0]** is unsigned integer.
4. **out_valid** should be low and **out** should be set to zero after initial reset.
5. **out_valid** should be set to high when output value is valid.
6. All outputs are synchronized at clock *positive* edge.
7. Test pattern will check whether your answer is correct or not at clock **negative edge** when **out_valid** is high.

Output Signals	Bit Width	Description
out	36	output result
out_valid	1	high when out is valid

Specifications

1. Top module name : **Online_test1** (File name : **Online_test1.v**)
2. Input pins: **clk** , **rst_n** , **in_valid** , **in[15:0]**, **in_mode**.
3. Output pins: **out_valid** , **out[35:0]**.
4. **out_valid** should not be raised when **in_valid** is high (when **in** data is transferring).
5. It is **active-high synchronous** reset.
6. The latency of your design in each pattern should not be larger than 1000 cycles.

Block Diagram

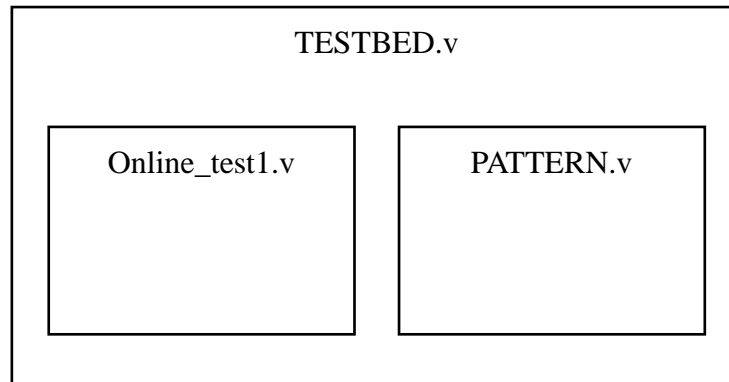

Note

1. Simulation step:
 - Put your design in 01_RTL
 - Simulation to check design : ./01_run.f
 - Show wave to debug: nWave &
 - Go to folder 02_SYN/ and check synthesis : ./01_run_dc
 - Clear up : ./09_clean_up
2. Please add your student ID and name to the file name of .v file before upload file on e3 platform:
Online_test1_0556123_陳小明.v
3. Sample waveform:

